

Chicago Hawaii ASIC, Multi-Purpose [CHAMP] Overview: Hawaii Designs

Presented by: Mike Cooney

On behalf of:

Matt Andrew, Wei Cai, Kurtis Nishimura, Larry
Ruckman, Gary Varner

Outline

- Background
- Hawaii Designs:
 - CSA
 - DAC
 - 2nd State Storage Array
 - D Flip-Flop
 - Voltage Controlled Delay Line
 - Waveform sampler
 - LVDS receiver
- Future


Background

- CHAMP ASIC
 - Joint U of Chicago and U of Hawaii test structure submission
 - Lays groundwork for future submissions
- Process: IBM 130nm
- First time in Hawaii using IBM process
- First ASIC design experience for:
 - Larry, Matt, Kurtis, Wei

Charge Sensitive Amplifier (CSA)

- Designed by Wei Cai
- Design goals:
 - 4ns rise time
- Overall dimensions:
 - 100 μ m wide by 112 μ m tall


CSA: Layout

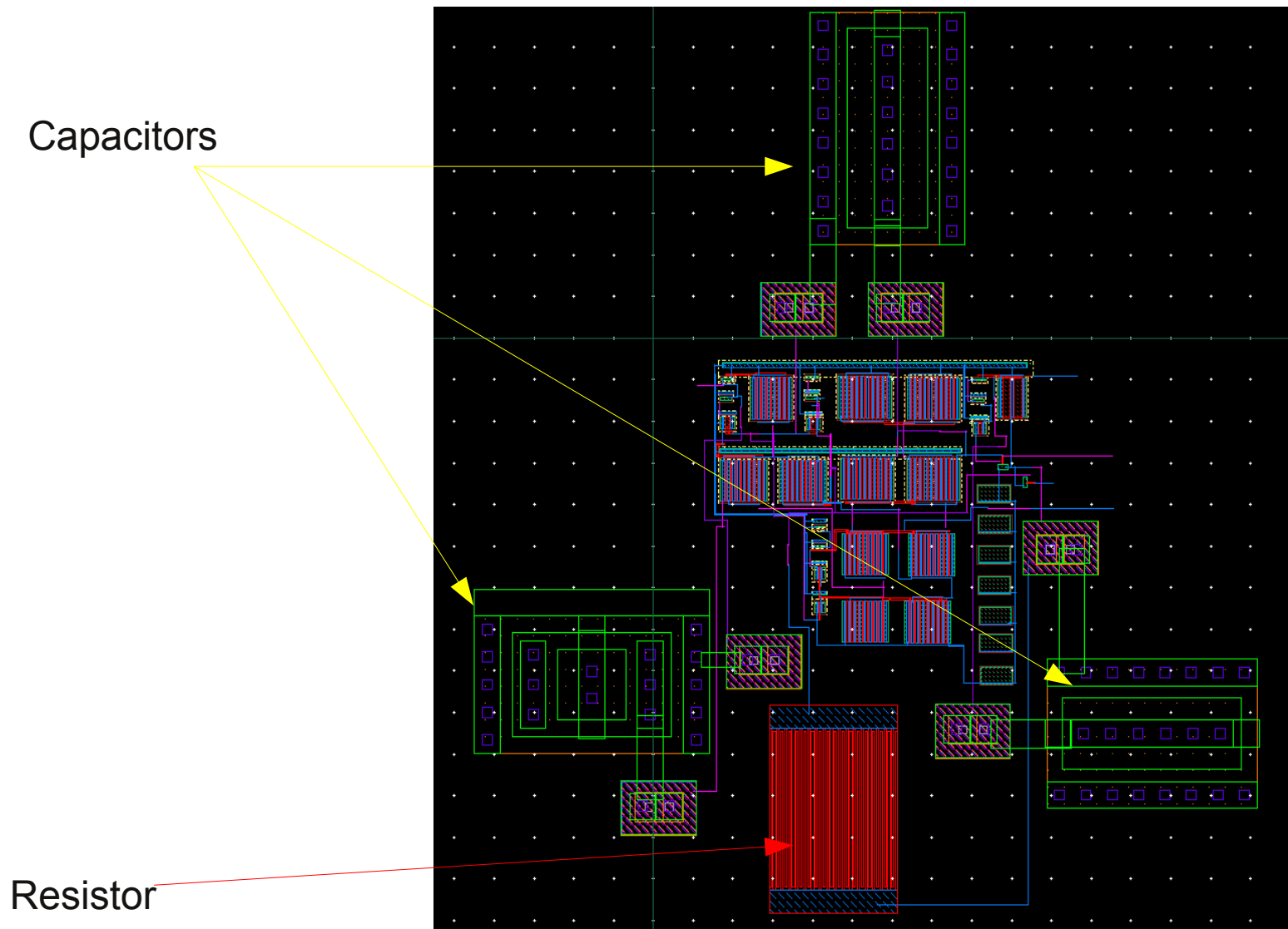

DAC

- Designed by Larry Ruckman
- Digital to Analog Converter:
 - R/2R design with SPI Interface
 - 12 bit resolution
 - 129.07 μm by 51.23 μm
 - Uses 1176 transistors
 - 6 external pins

DAC: 12 Bit Simulation

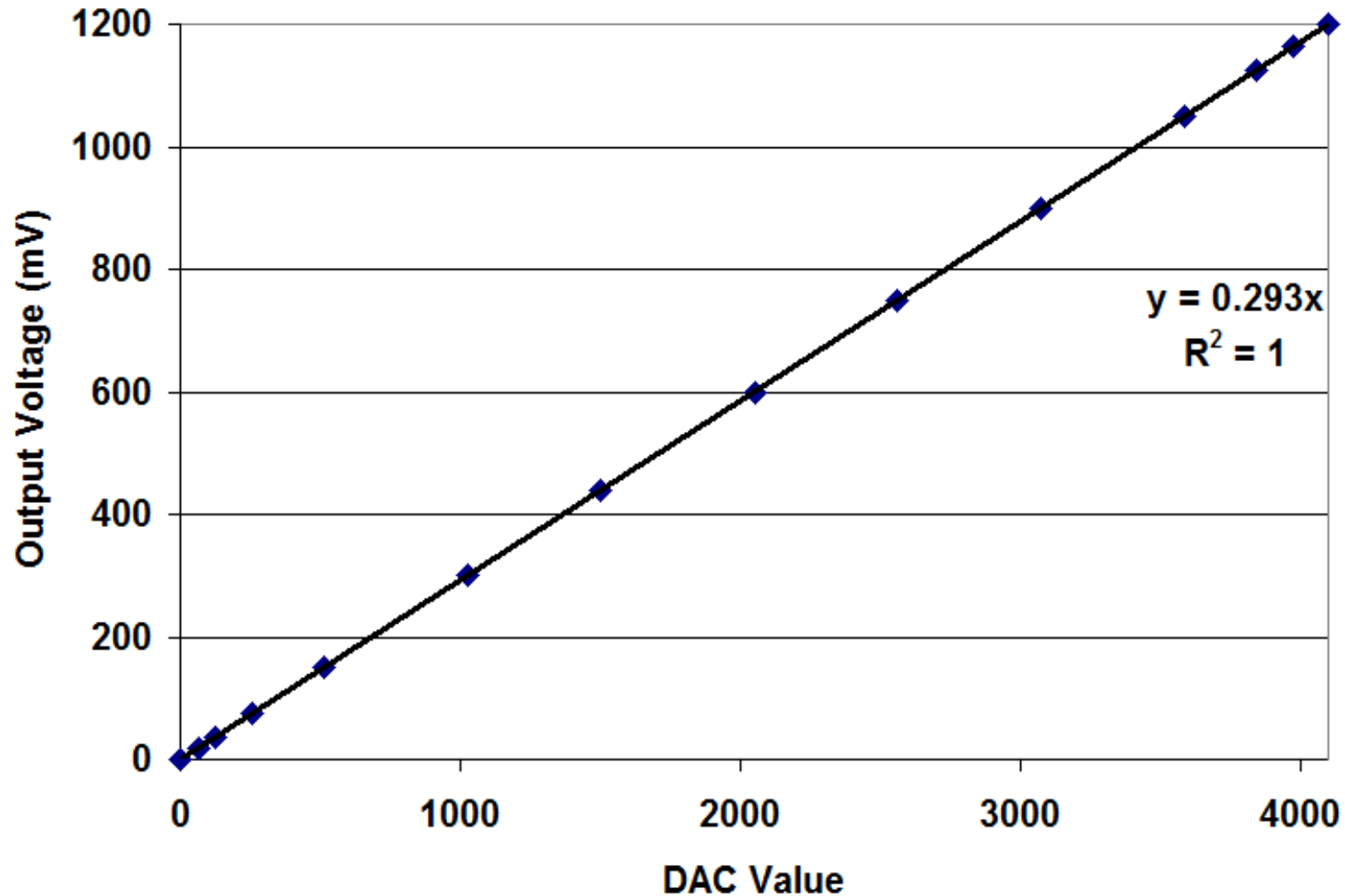


- $\text{LSB} = (1.2 \text{ V}) / (2^{12}) = 293 \text{ mV/count}$
- Theoretical slope agrees with simulation
- Slope errors in measurement will come from fabrication tolerances/errors

2nd Stage Storage Array


- Designed by Larry Ruckman
- Designed to perform long term storage (~ms) while avoiding large leakage currents as a second stage Wilkinson storage array.
- Uses large storage capacitors (1pF) with a differential pair.

Storage Array: Schematic

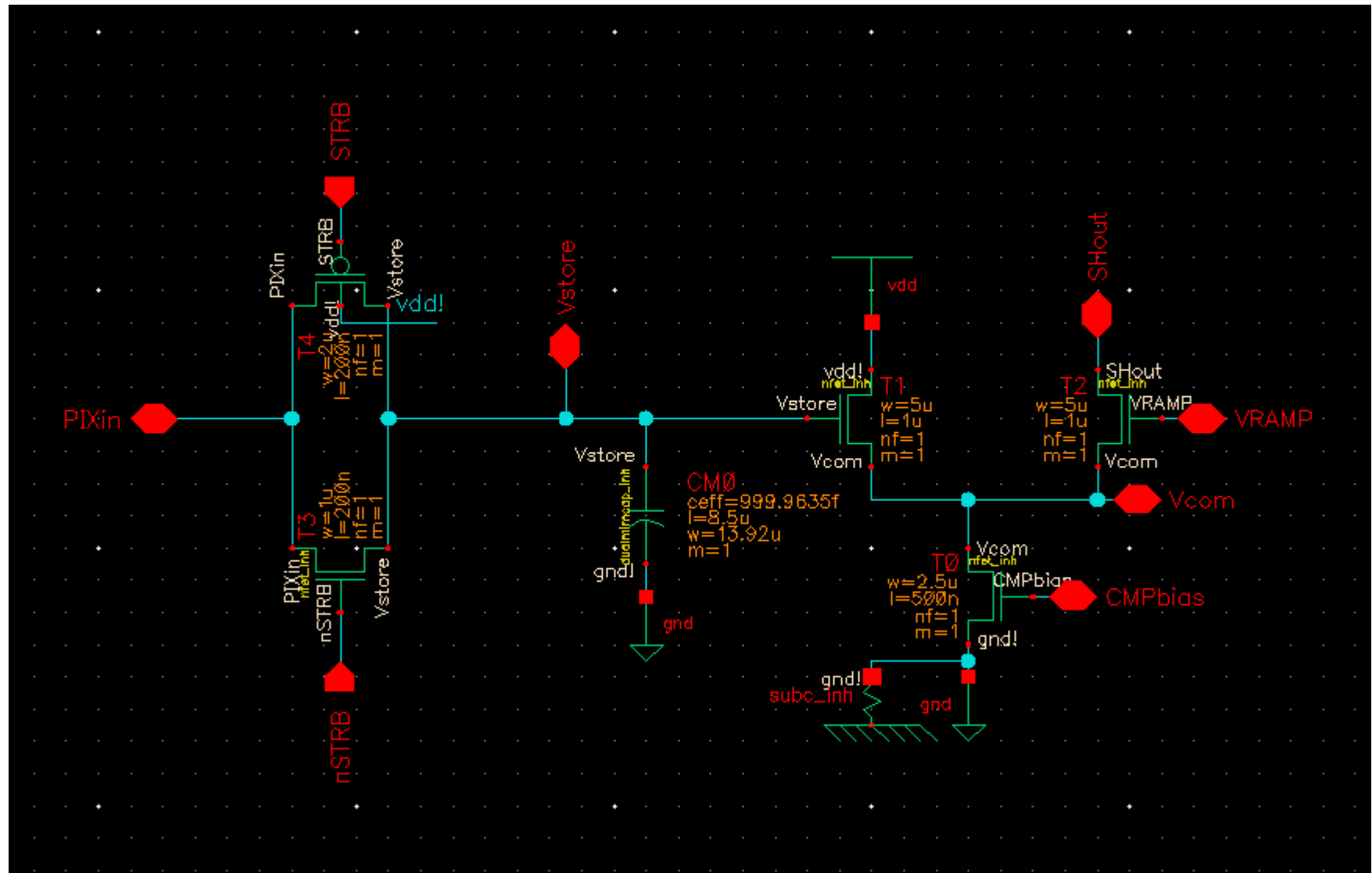

Storage Array: Layout

 - 138.11 μm by 135.33 μm
- Includes address decoding, 16 cells
- Possibly a solution for deep storage in a future waveform ASIC designs in this process



D Flip Flop

- Designed by Matt Andrew
- Two designs:
 - NOR gates:
 - Simulates operation at 2.15GHz
 - Possibly up to 2.5GHz operation
 - NOR + NAND gates:
 - Simulates operation at 3.5GHz
 - 40μm by 26μm


Voltage Controlled Delay Lines

- Designed by Matt Andrew
- Two delay lines
 - 64 stages with 9 stage delay
 - One delay line uses normal voltage FETs
 - One delay line uses low voltage FETs
- One ring oscillator
 - 11 stages with 9 stage delay
 - Several GHz in simulation (parasitics)

VCDL: Layout

Normal Vth VCDL

Low Vth VCDL

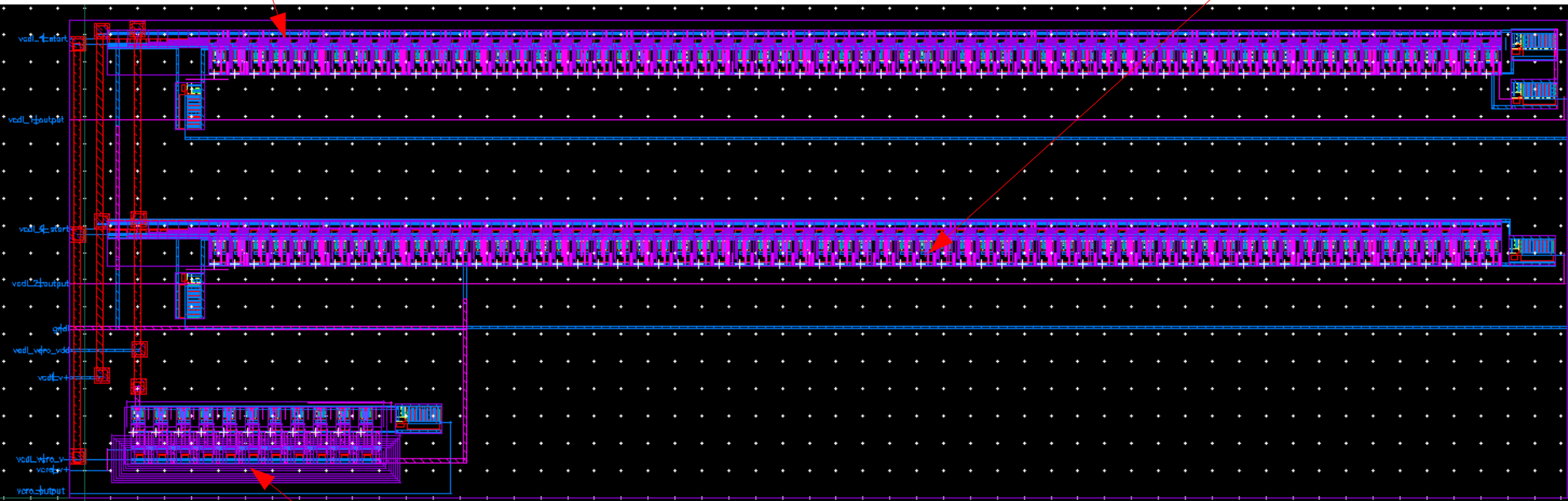


Ring oscillator

Waveform Sampling Arrays


Four sampling arrays to explore high analog bandwidth sampling, compare simulated / measured bandwidth.

Simulated bandwidths (approximate): **1.8, 2.2, 2.6, 4.2 GHz**

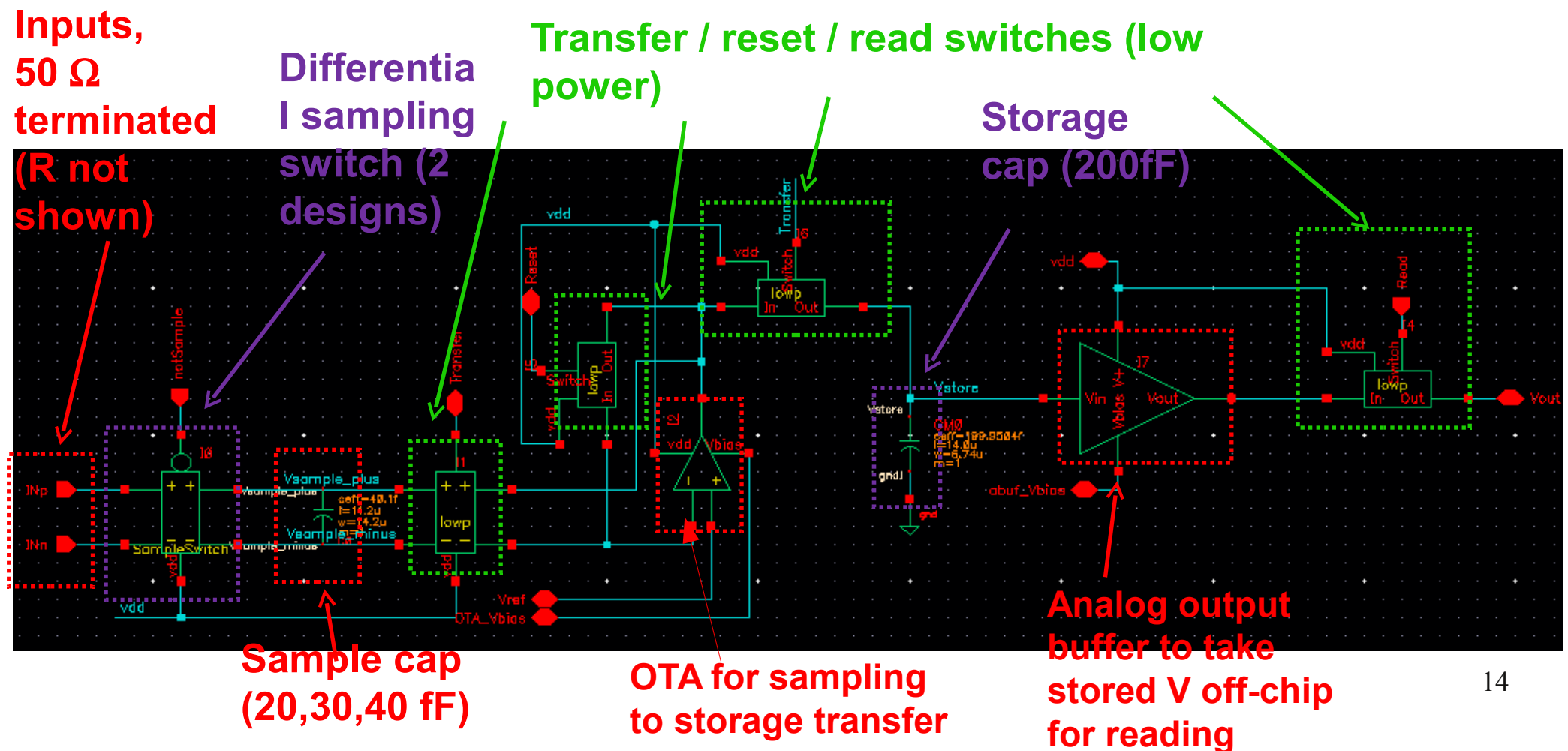Each sampling cell consists of 64 of the following basic cell:



Waveform Sampling: Layout

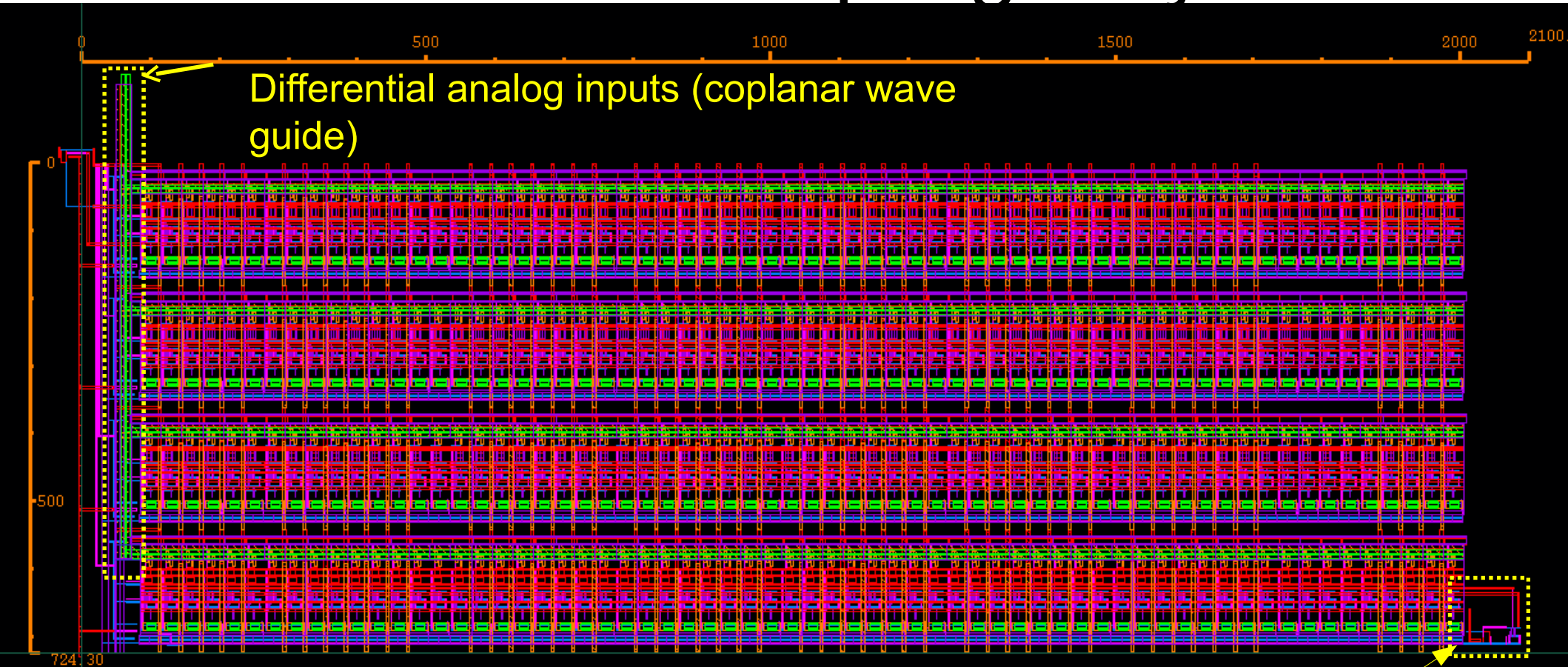

For each array:

- Delay line sits above to generate sampling
- Shift register sits below to control the read signals.
- Enable logic allows each array to be turned off/on for independent testing.


Independent test structures:

- OTA
- Analog output buffer

LVDS Receiver

- Designed by Mike Cooney
- A Low Voltage Differential Receiver
 - Translates 2.5V I/O to core 1.2V
 - Simulates operation at 1+ GHz
 - 100mV signal differential
 - 57 μ m wide by 47 μ m tall

LVDS Receiver: Layout

 

Conclusion

- May submission in IBM 130nm lays groundwork for future designs
 - High speed serial I/O interfaces (LVDS)
 - Deep sampling capability
 - Trim DACs for bias control
- First ASIC design experience for 4/5 Hawaii users